

More Efficient Design

- ❑ Use already available arithmetic circuit and incorporate logical operations
- ❑ Procedure
 - Design the arithmetic section independently
 - Take the circuit, consider $C_{in} = 0$, and determine which logic operations are automatically generated from the arithmetic circuit
 - Modify the circuit to incorporate required but not automatically generated logic operations



More Efficient Design

- Use already available arithmetic circuit and incorporate logical operations

s_1	s_0	Y_i
0	0	0
0	1	B_i
1	0	B'_i
1	1	1

s_1	s_0	X_i	Y_i
0	0	A_i	0
0	1	A_i	B_i
1	0	A_i	B'_i
1	1	A_i	1

Required
operation

OR
XOR
AND
NOT



More Efficient Design

- Use already available arithmetic circuit and incorporate logical operations

s_1	s_0	Y_i
0	0	0
0	1	B_i
1	0	B'_i
1	1	1

$s_2 = 0 \rightarrow$ arithmetic

$s_2 = 1 \rightarrow$ logical

Logical part & $C_{in} = 0$

$$A \oplus B$$

$C_{in} = 1$ দিলে

$$A \oplus B \oplus 1 = \text{not এর যোগ্য}$$

s_2	s_1	s_0	X_i	Y_i	C_i	$F_i = X_i \oplus Y_i$	Operation	Required operation
1	0	0	A_i	0	0	$F_i = A_i$	Transfer A	OR
1	0	1	A_i	B_i	0	$F_i = A_i \oplus B_i$	XOR	XOR
1	1	0	A_i	B'_i	0	$F_i = A_i \odot B_i$	Equivalence (X-NOR)	AND
1	1	1	A_i	1	0	$F_i = A'_i$	NOT	NOT

$$x \oplus y \oplus z$$

↑

0 দিলে

$$= x \oplus y$$

$$A \oplus \bar{B}$$

$$= AB + \bar{A}\bar{B}$$

Incorporating remaining functions

□ Unresolved cases

s_2	s_1	s_0	X_i	Y_i	Automatically Obtained F_i	Required F_i
1	0	0	A_i	0	$F_i = A_i$	$F_i = A_i + B_i$
1	1	0	A_i	B'_i	$F_i = A_i \odot B_i$	$F_i = A_i B_i$

এই control bit এর জন্য i/p ই $A+B$ দিবে

$$(A+B) \oplus 0 = A+B$$

$$X = A + s_2 \overline{s_1} \overline{s_0} B$$

$$o/p \rightarrow AB \oplus \overline{B}$$

$$= \overline{A} \overline{B} \overline{B} + A B \cdot B$$

$$= (\overline{A} + \overline{B}) \overline{B} + AB = \overline{A} \overline{B} + AB + \overline{B}$$



2nd case 4:

$$(A + K) \oplus \overline{B} = AB$$

↓ A এর সাথে এক্সক্লুসিভ যোগ করবো হেন AB চলে আসবে।

$$= \overline{(A+K)} \overline{B} + (A+K)B = \overline{A} K \overline{B} + AB + KB$$

$$K \text{ यदि } \overline{B} \text{ হয়} \rightarrow \overline{A} B \overline{B} + A B + B \overline{B} = AB$$

s_2	s_1	s_0	X_i	Y_i	Automatically Obtained F_i	Required F_i
			A_i	0	$F_i = A_i$	$F_i = A_i + B_i$
			A_i	B_i'	$F_i = A_i \odot B_i$	$F_i = A_i B_i$

$$X = A + s_2 \overline{s_1} \overline{s_0} B + s_2 s_1 \overline{s_0} \overline{B}$$

Incorporating remaining functions

From Table 9-3, we see that when $s_2 = 1$, the input carry C_i in each stage must be 0. With $s_1 s_0 = 00$, each stage as it stands generates the function $F_i = A_i$. To change the output to an OR operation, we must change the input to each full-adder circuit from A_i , to $A_i + B_i$. This can be accomplished by ORing B_i and A_i when $s_2 s_1 s_0 = 100$.

The other selection variables that give an undesirable output occur when $s_2 s_1 s_0 = 110$. The unit as it stands generates an output $F_i = A_i \odot B_i$ but we want to generate the AND operation $F_i = A_i B_i$. Let us investigate the possibility of ORing each input A_i with some Boolean function K_i . The function so obtained is then used for X_i when $s_2 s_1 s_0 = 110$:


$$F_i = X_i \oplus Y_i = (A_i \oplus K_i) \oplus B'_i = A_i B_i + K_i B_i + A'_i K'_i B'_i$$

(A + K)

Careful inspection of the result reveals that if the variable $K_i = B'_i$, we obtain an output:

$$F_i = A_i B_i + B'_i B_i + A_i B_i B'_i = A_i B_i$$

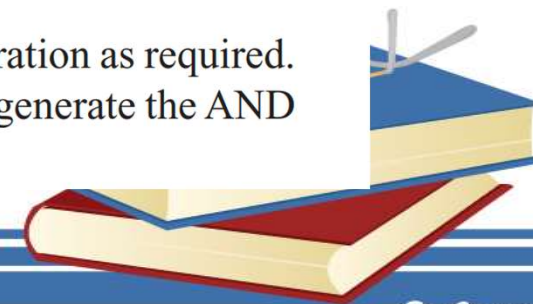Two terms are equal to 0 because $B_i B'_i = 0$. The result obtained is the AND operation as required. The conclusion is that, if A_i is ORed with B'_i when $s_2 s_1 s_0 = 110$, the output will generate the AND operation.



Final Boolean Functions

- Combining the arithmetic and logical cases, we get the final form of the Boolean function as:

$$X_i = A_i + s_2 s_1' s_0' B_i + s_2 s_1 s_0' B_i'$$




$$Y_i = s_0 B_i + s_1 B_i'$$

$$Z_i = s_2' C_i$$

↳ logical operation এর
সময় যেন $z_i = 0$ রফে
যায়।

→ প্রতি bit এর জন্য

Selection				Output	Function
s_2	s_1	s_0	C_{in}		
0	0	0	0	$F = A$	Transfer A
0	0	0	1	$F = A + 1$	Increment A
0	0	1	0	$F = A + B$	Addition
0	0	1	1	$F = A + B + 1$	Add with carry
0	1	0	0	$F = A - B - 1$	Subtract with borrow
0	1	0	1	$F = A - B$	Subtraction
0	1	1	0	$F = A - 1$	Decrement A
0	1	1	1	$F = A$	Transfer A
1	0	0	X	$F = A \vee B$	OR
1	0	1	X	$F = A \oplus B$	XOR
1	1	0	X	$F = A \wedge B$	AND
1	1	1	X	$F = \bar{A}$	Complement A

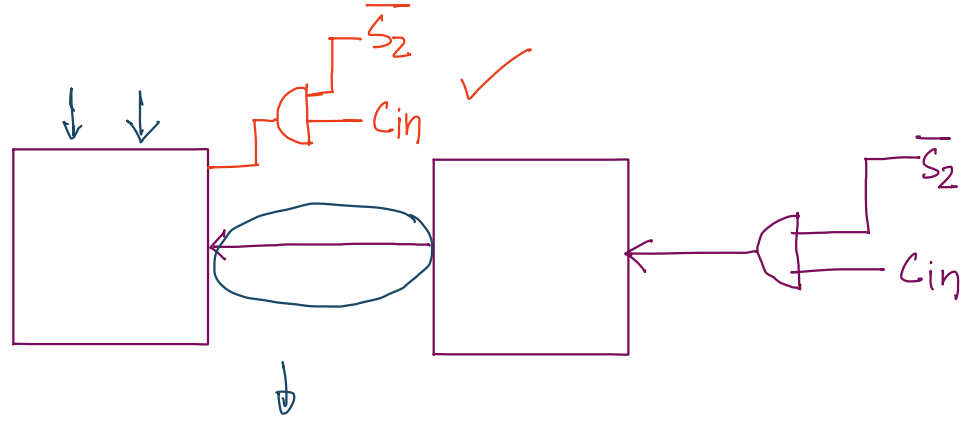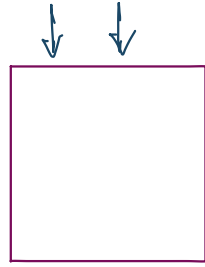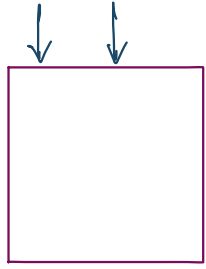

করা যাবে না।

logically $Cin = 0$ হওয়া লাগবে অবশ্যই।

লি টে

$\left. \begin{matrix} x_i \\ y_i \\ z_i \end{matrix} \right\}$ যেখানে box দেওয়া থাকবে সেখানে
 final expression লেখা লাগবে।

Let's See Another Example

- Derive the input equations (X_i , Y_i and Z_i) for the parallel adders to be used in the ALU which satisfies the following functional design specification.

s_2	s_1	c_{in}	Required Functions
0	0	0	$F = AB + C$
0	0	1	$F = AB + C + 1$
0	1	0	$F = AB$
0	1	1	$F = AB + 1$
1	0	x	$F = (AB)'$
1	1	x	$F = AB$



arithmetic এ
এই দুটো
consider করবো না।

s_2	s_1	C_{in}
0	0	0
0	0	1
0	1	0
0	1	1
1	0	X
1	1	X

X	Y	Z
AB	C	0
AB	C	1
AB	0	0
AB	0	1
AB	C	X
AB	0	X

Required Function

$$AB + C$$

$$AB + C + 1$$

$$AB$$

$$AB + 1$$

$$F = (AB)'$$

$$F = AB$$

এগুলো বানাতে যা যা
লাগবে যেটাই x, y, z
এ লিখবো।

logical এর জন্য $s_2 = 1$

$s_1 = 0$ তে $Y = C$ } arithmetic এ
 $s_1 = 1$ এ $Y = 0$ } দেখেছি।

$$AB \oplus C \rightarrow (AB)'$$

অর্থাৎ যখন 1 দাঁড়াতে হবে এই control bit
এর জন্য।

s_2 তা add করে দিলেই হবে,

arithmetic

$$X = AB$$

$$Y = \overline{s_1} C$$

$$Z = C_{in} \overline{s_2}$$

logical

$$X = AB$$

$$Y = s_2 \overline{s_1}$$

$$Z = \overline{s_2} C_{in}$$

Finally

$$X = AB$$

$$Y = \overline{s_1} C + s_2 \overline{s_1}$$

$$Z = \overline{s_2} C_{in}$$

Solution

S_2	S_1	C_{in}	X	Y	Z	Required Functions
0	0	0	AB	C	0	$F = AB + C$
0	0	1	AB	C	1	$F = AB + C + 1$
0	1	0	AB	0	0	$F = AB$
0	1	1	AB	0	1	$F = AB + 1$
1	0	x	AB	1	x	$F = (AB)'$
1	1	x	AB	0	x	$F = AB$



Solution

□ $X = AB$

□ $Y = s_1' C$

□ $Z = s_2' c_{in}$

□ Then for logical operations,

➤ $X = AB$

➤ $Y = s_1' C + s_2 s_1'$

➤ $Z = s_2' c_{in}$

