 


Combinational Elements



Storage Element: Reg File

- Register File consists of 32 registers

- Two 32 bit output busses

- busA and busB

- One 32 bit input bus

- busW

- Register 0 hard wired to value 0

- Register selected by

- RA selects register to put on busA

- RB selects register to put on busB

- RW selects register to be written via busW when Write Enable is 1


- Clock input (CLK)

- CLK input is a factor only for write operation

- During read, behaves as combinational logic block

- RA or RB stable \Rightarrow busA or busB valid after "access time"

- Minor simplification of reality

 

Storage Element: Memory


■ Memory

- One input bus: Data In
- One output bus: Data Out
- Address selection

- Address selects the word to put on Data Out
- To write to address, set Write Enable to 1

■ Clock input (CLK)

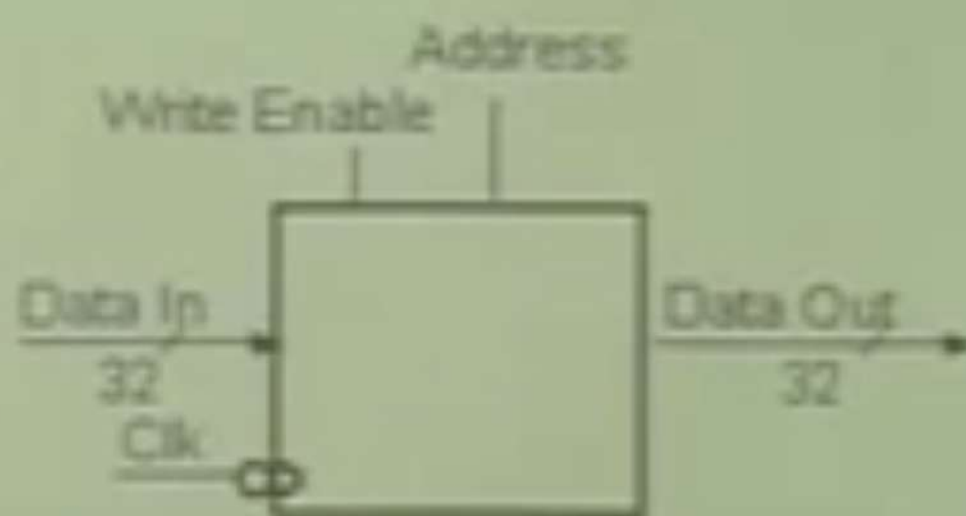
- CLK input is a factor only for write operation
- During read, behaves as combinational logic block
 - Valid Address \Rightarrow Data Out valid after "access time"
 - Minor simplification of reality




Some Logic Design...

- All storage elements have same clock
 - Edge-triggered clocking
 - "Instantaneous" state change (simplification!)
 - Timing always work if the clock is slow enough

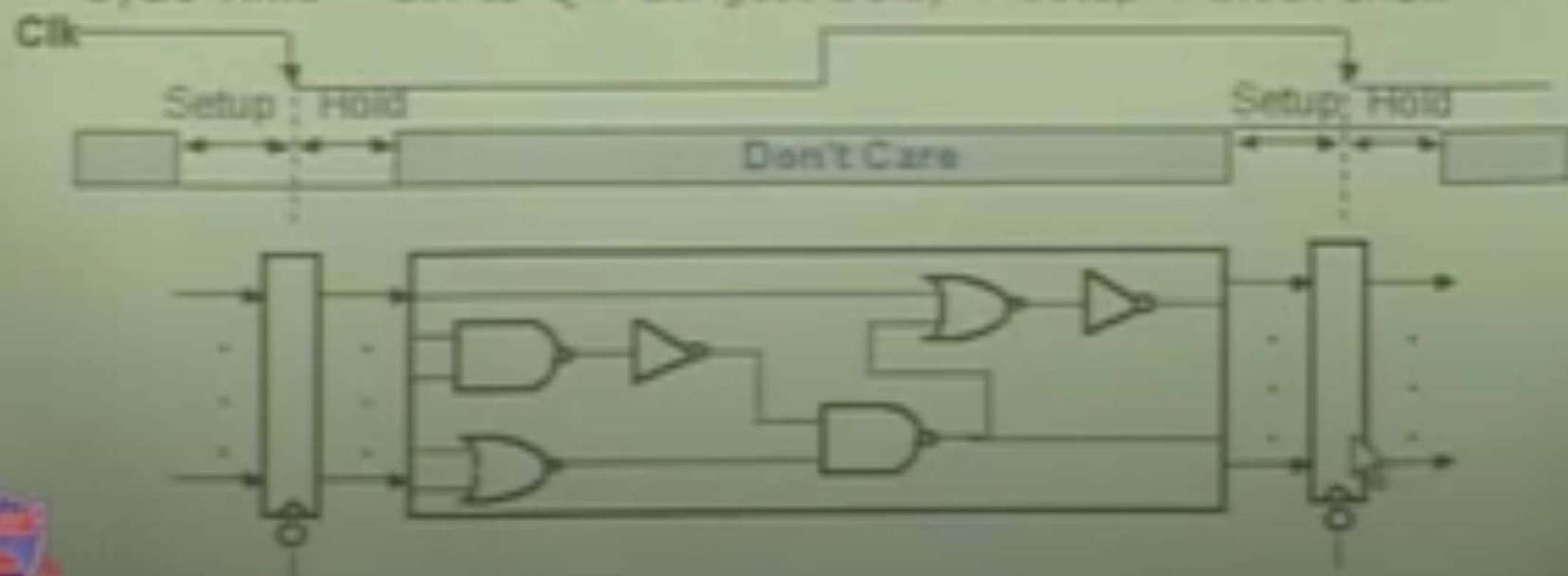Cycle Time = Clk-to-Q + Longest Delay + Setup + Clock Skew



Datapath: IF Unit

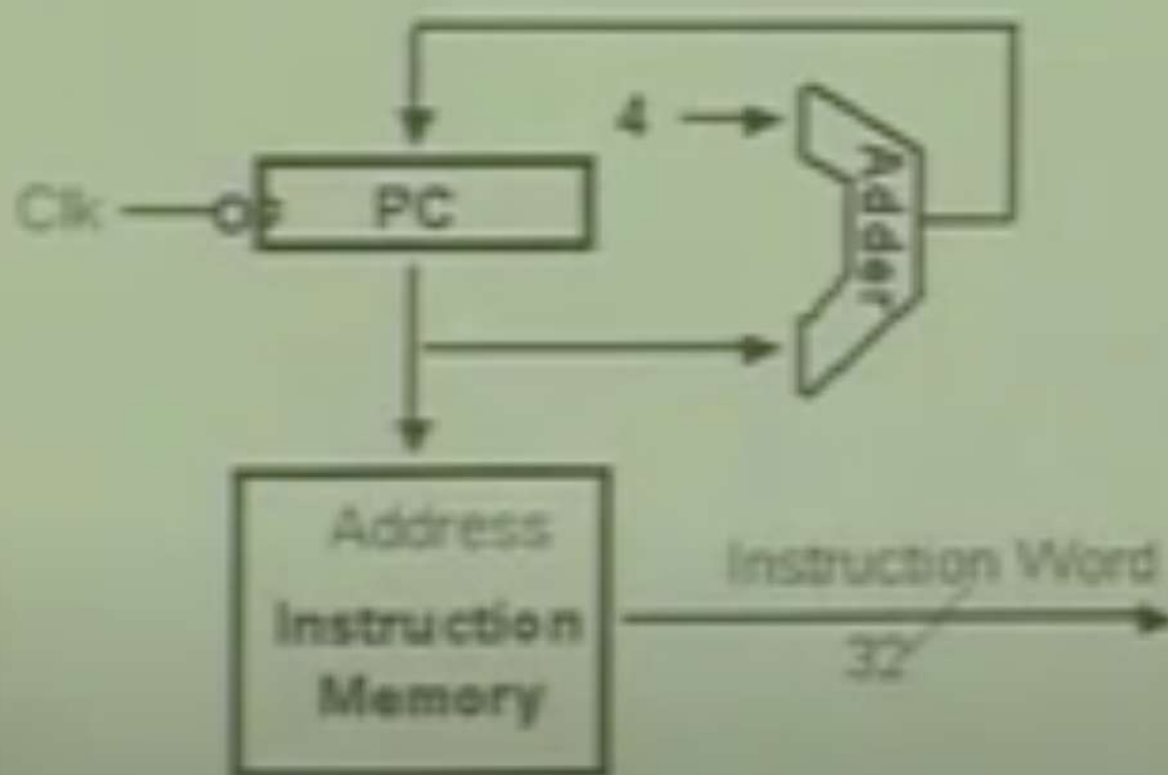

Add RTL

■ Add instruction

`add rd, rs, rt`

`Mem[PC] :`

`R[rd] <- R[rs] + R[rt] :`

`PC <- PC + 4 :`

Fetch instruction from memory

Add operation

Calculate next address

Bits

6

5

5

5

5

6

OP=0

rs

rt

rd

sa

funct

first
source
register

second
source
register

result
register

shift
amount

function
code
(-PC)

Sub RTL

■ Sub instruction

sub rd, rs, rt

Mem[PC] :

R[rd] ← R[rs] - R[rt] :

PC ← PC + 4 :

Fetch instruction from memory

Sub operation

Calculate next address

Bits

6

5

5

5

5

6

OP=0

rs

rt

rd

sa

funct

first
source
register

second
source
register


result
register

shift
amount

function
code
(-31)

Datapath: Reg/Reg Ops

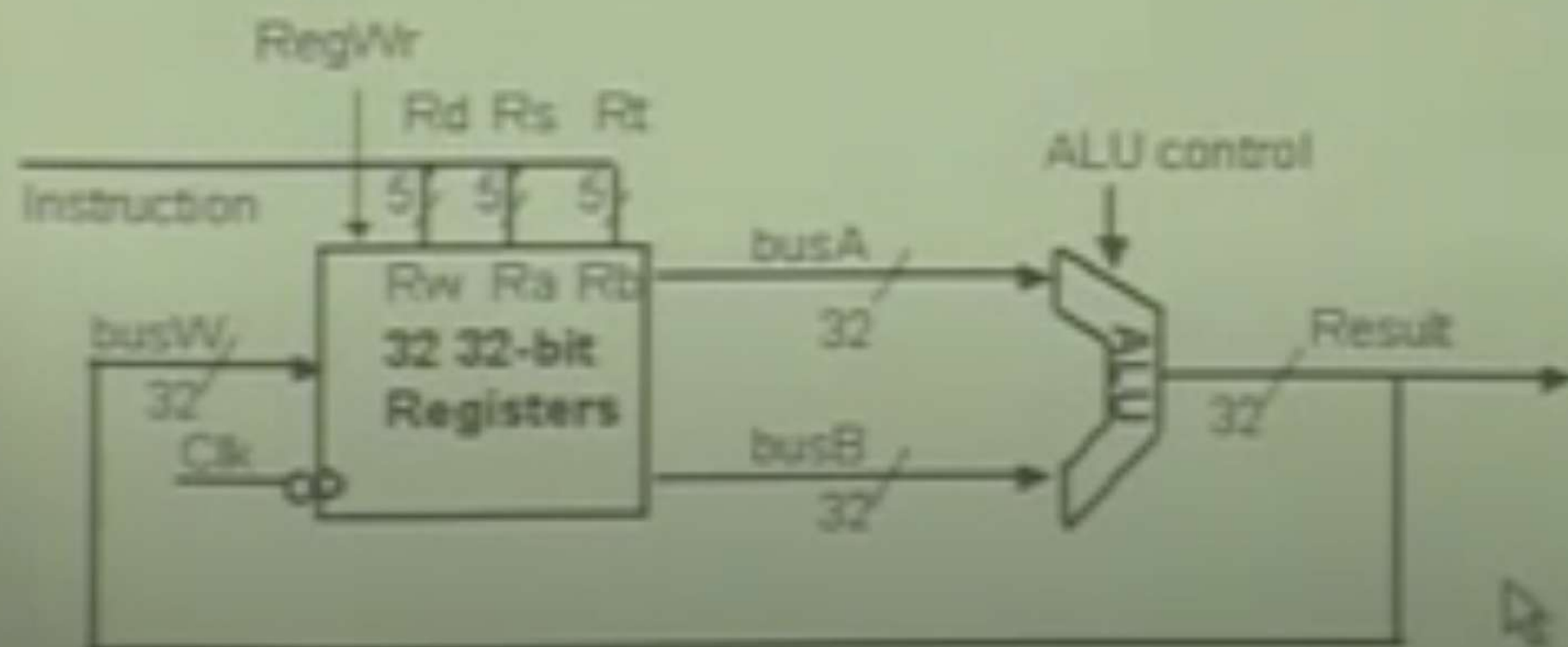- $R[rd] \leftarrow R[rs] \text{ op } R[rt];$
 - ALU control and RegWr based on decoded instruction
 - Ra, Rb, and Rd from rs, rt, rd fields



OR Immediate RTL

■ OR Immediate instruction

`ori rt, rs, imm`

`Mem[PC] :`

Fetch instruction from memory


`R[rt] ← R[rs] OR ZeroExt(imm) :`

OR operation with Zero-Extend

`PC ← PC + 4 :`

Calculate next address

Bits

 


first source register
second register (dest)

immediate

Datapath: Immediate Ops

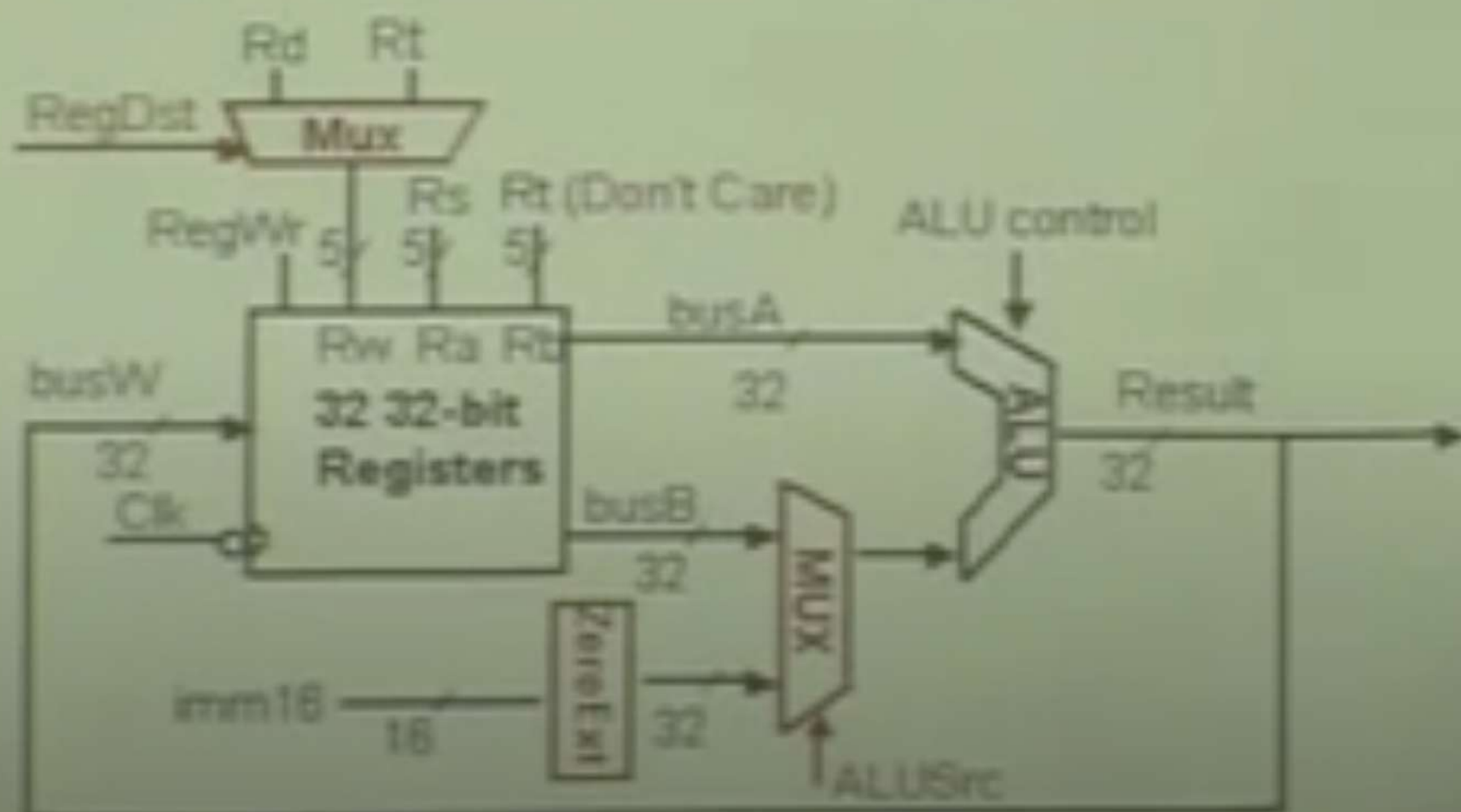- Rw set by MUX and ALU B set as busB or ZeroExt(imm)
- ALUSrc and RegDst set based on instruction



Load RTL

■ Load instruction

`lw rt, rs, imm`

`Mem[PC] :`

Fetch instruction from memory

`Addr <- R[rs] + SignExt(imm) :`

Compute memory addr

`R[rt] <- Mem[Addr] :`

Load data into register

`PC <- PC + 4 :`

Calculate next address

Bits

6

5

5

16




first
source
register

second
register
(dest)

immediate

Datapath: Load

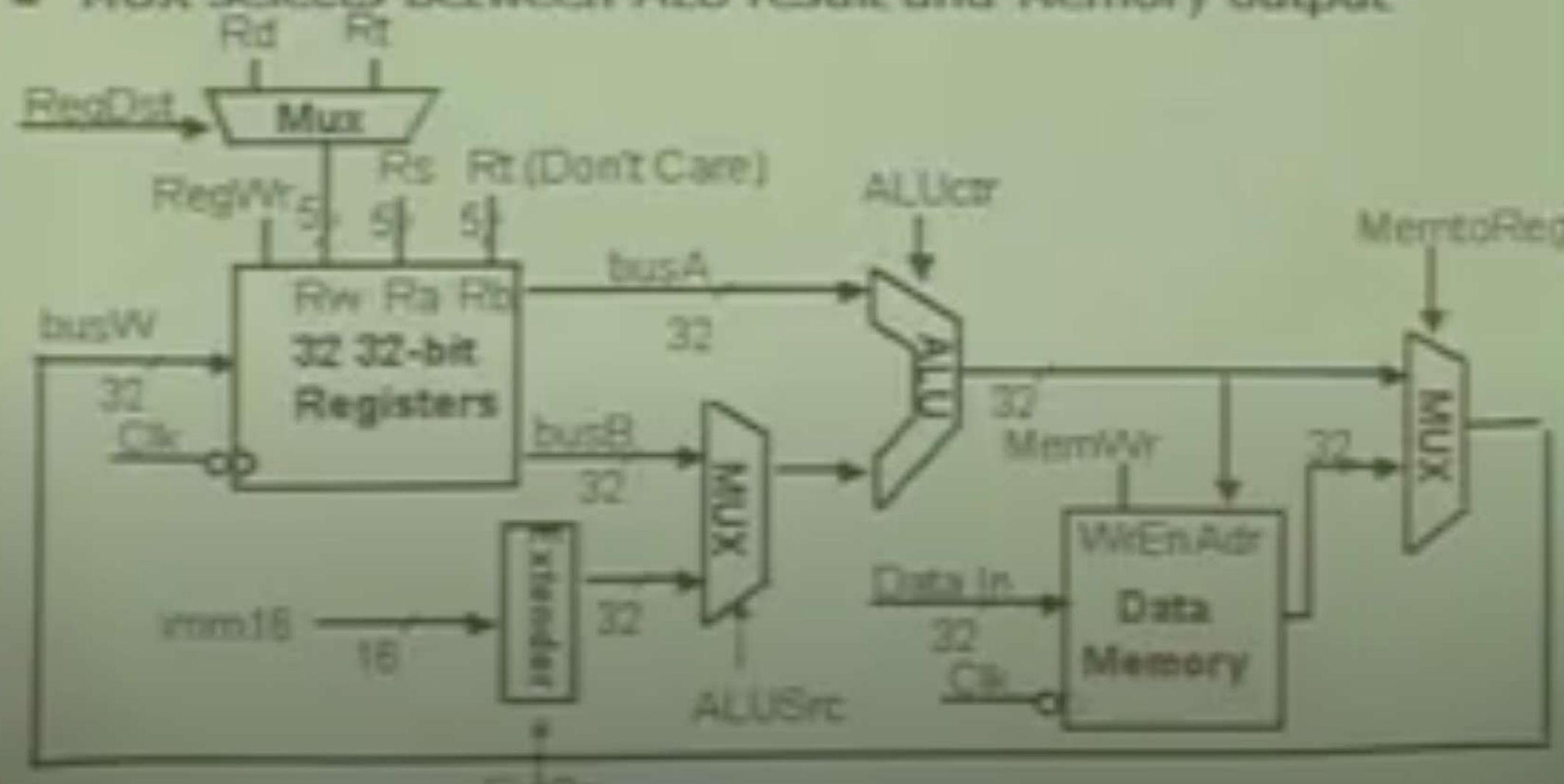- Extender handles sign vs. zero extension of immediate
- MUX selects between ALU result and Memory output




Store RTL

■ Store instruction

sw rt, rs, imm

Mem[PC] :	Fetch instruction from memory
Addr \leftarrow R[rs] + SignExt(imm) :	Compute memory addr
Mem[Addr] \leftarrow R[rt] :	Load data into register
PC \leftarrow PC + 4 :	Calculate next address

Bits

 


first
source
register

second
source
register

immediate

Datapath: Store

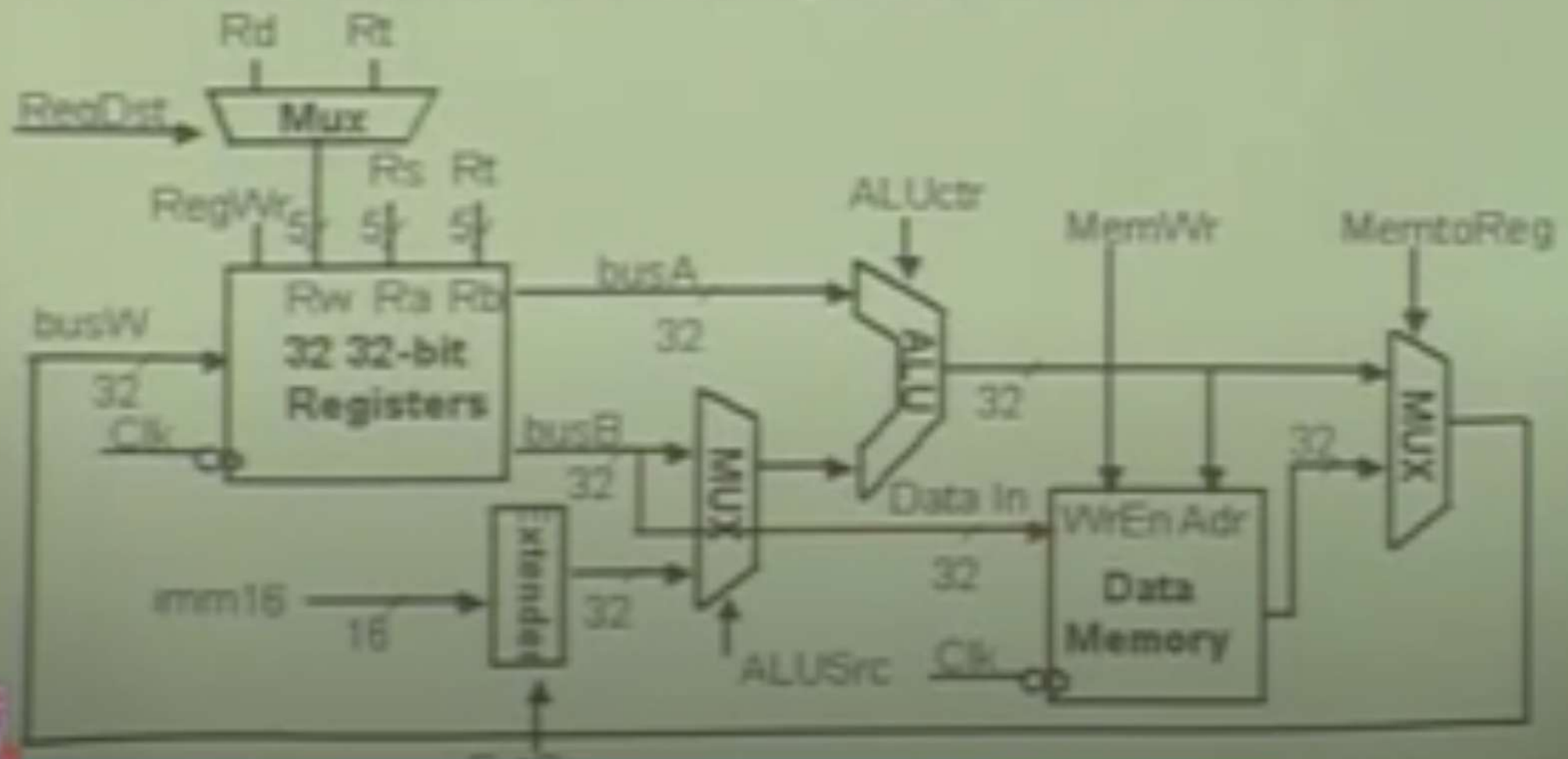- Register *rt* is passed on busB into memory
- Memory address calculated just as in *lw* case



Branch RTL

■ Branch instruction

beq rs, rt, imm

Mem[PC]:

Fetch instruction from memory

Cond \leftarrow R[rs] - R[rt]:

Calculate branch condition

if (Cond eq 0)

Test if equal

PC \leftarrow PC + 4 +


SignExt(imm) * 4; Calculate PC Relative address

else

PC \leftarrow PC + 4;

Calculate next address

Bits

 

first
source

second
source

immediate

Datapath: Branch

